

# CSM51A Discussion #6

Hyunjin Kim

# Outline

- Review HW5
- Chapter 8
  - Timing Parameters of Flipflops
- Chapter 7
  - Mealy vs. Moore machine
  - State transition table
  - State Diagram
  - State Minimization


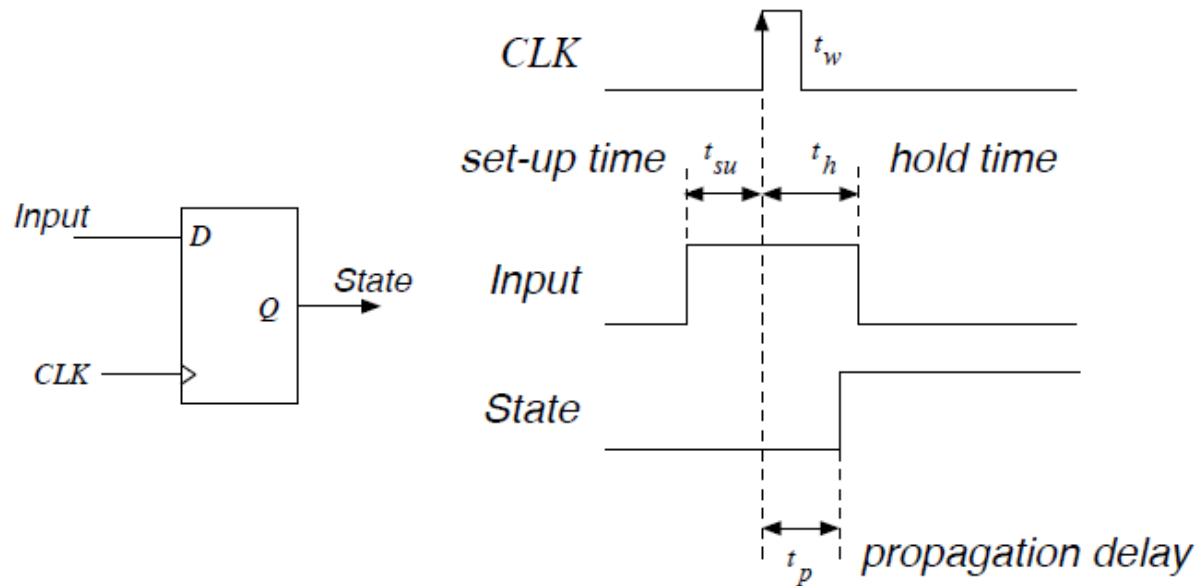


Figure 8.12: TIME BEHAVIOR OF CELL.

Violation of set-up time or hold time causes a **undefined** output.

# Example

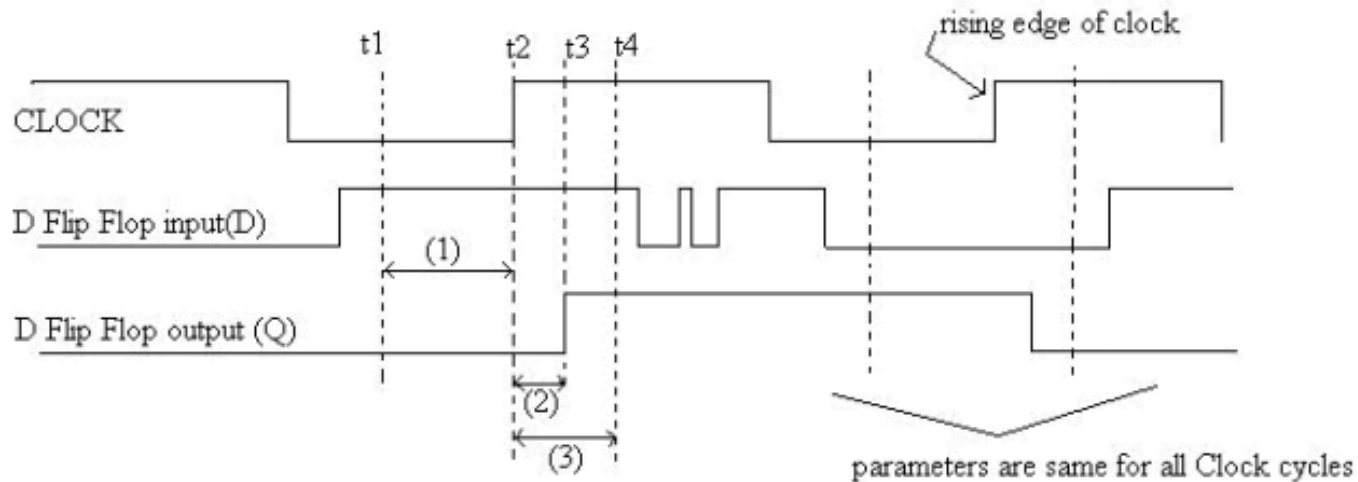

- (1) the **Setup Time**  $[t_2 - t_1]$ : the minimum amount of time Input must be held constant BEFORE the clock tick.
- (2) the **Propagation delay** of the Flip Flop  $[t_3 - t_2]$ : this is the time that it takes for the new input to be to propagate and influence the output.
- (3) the **Hold time**  $[t_4 - t_2]$ : the minimum amount of time the Input is held constant AFTER the clock tick: Most current FF has **zero** (negative) hold time

## Mealy machine

$$z(t) = H(s(t), x(t))$$

$$s(t + 1) = G(s(t), x(t))$$


## Moore machine

$$z(t) = H(s(t))$$

$$s(t + 1) = G(s(t), x(t))$$

- EQUIVALENT IN CAPABILITIES



# Mealy vs Moore

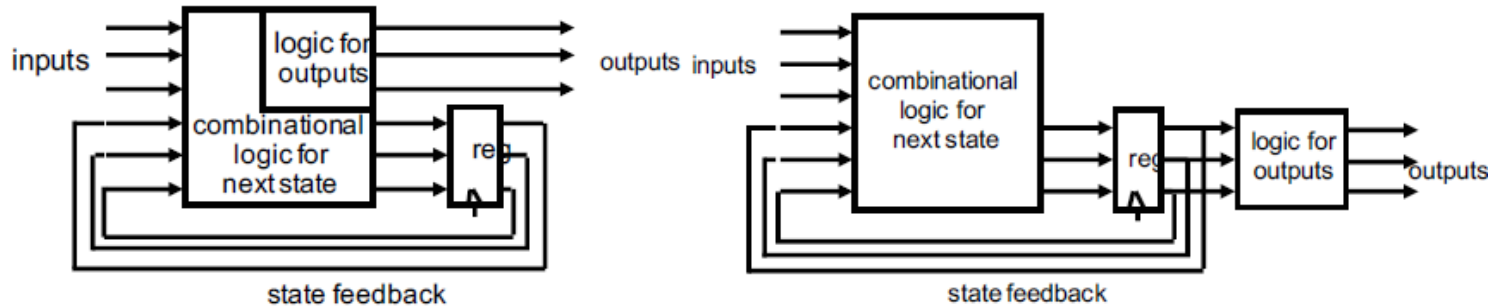

- Mealy
  - Less states
    - #output on arcs ( $n^2$ ) than states ( $n$ )
  - Input change can cause output change in a clock period -> X
- Moore
  - Usually more states than Mealy
  - Safer to use
    - Outputs change at clock edge

# Mealy vs Moore

- Example
  - "11" pattern detector

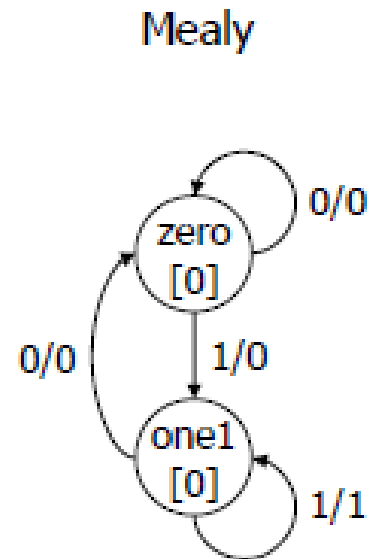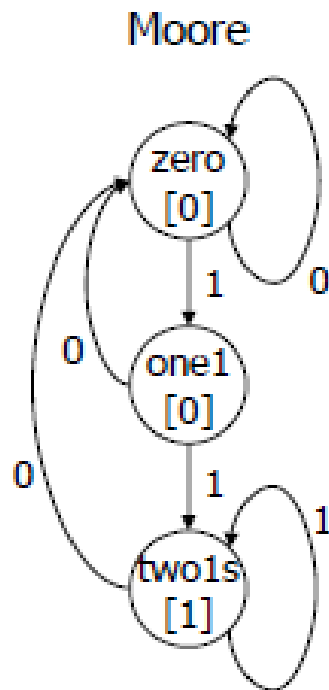

Ex7.1 A sequential system has one input with values a, b, and c and one output with values p and q. The output is q whenever the input sequence has an even number of a's and an odd number of b's. Obtain a state description of the system.

Input:

$$x(t) \in \{a, b, c\}$$

Output:

$$z(t) \in \{p, q\}$$

Function:

$$z(t) = \begin{cases} q & \text{if number of a's in } x(0, t-1) \text{ is even and number of b's is odd.} \\ p & \text{otherwise} \end{cases}$$

Initial state:

$$s_a(0) = 0$$

$$s_b(0) = 0$$

Transition function:


$$s_a(t+1) = \begin{cases} s_a(t)' & \text{if } x(t) = a \\ s_a(t) & \text{otherwise} \end{cases}$$

$$s_b(t+1) = \begin{cases} s_b(t)' & \text{if } x(t) = b \\ s_b(t) & \text{otherwise} \end{cases}$$



$PS$	Input			
	$x = a$	$x = b$	$x = c$	
(0,0)	(1,0)	(0,1)	(0,0)	p
(0,1)	(1,1)	(0,0)	(0,1)	q
(1,0)	(0,0)	(1,1)	(1,0)	p
(1,1)	(0,1)	(1,0)	(1,1)	p
	NS			Output ( $z$ )

Mealy or Moore?

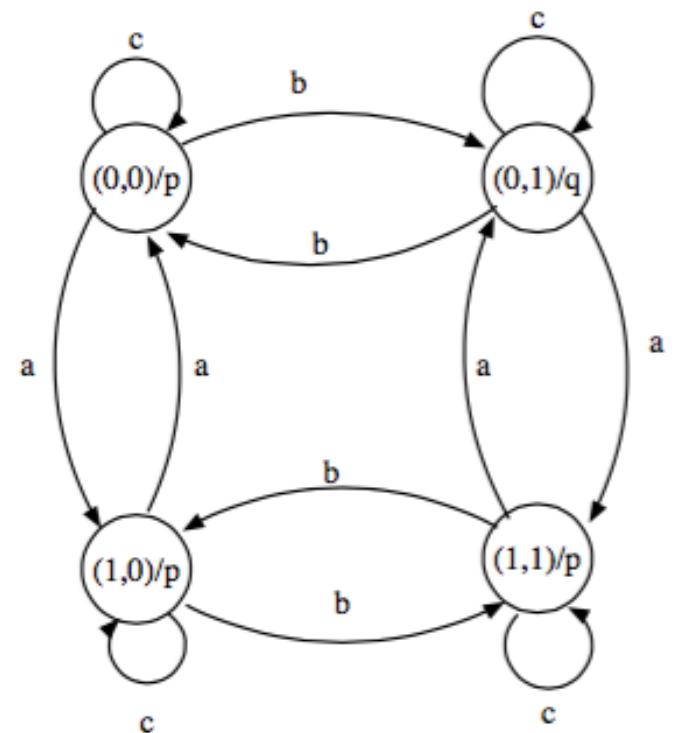

Ex7.5 Determine the state diagram for the sequential system described by the following expressions:


$$\begin{array}{lll} s(t+1) = & s(t) & \text{if } x=a \\ & (s(t)+1) \bmod 5 & \text{if } x=b \\ & 2 & \text{if } x=c \end{array}$$

$$\begin{array}{ll} z(t) = 0 & \text{if } s(t) \text{ is even} \\ & 1 \quad \text{if otherwise} \end{array}$$

The system has five states labeled 0, 1, 2, 3, and 4

Mealy or Moore?

# Ex7.5 Solution

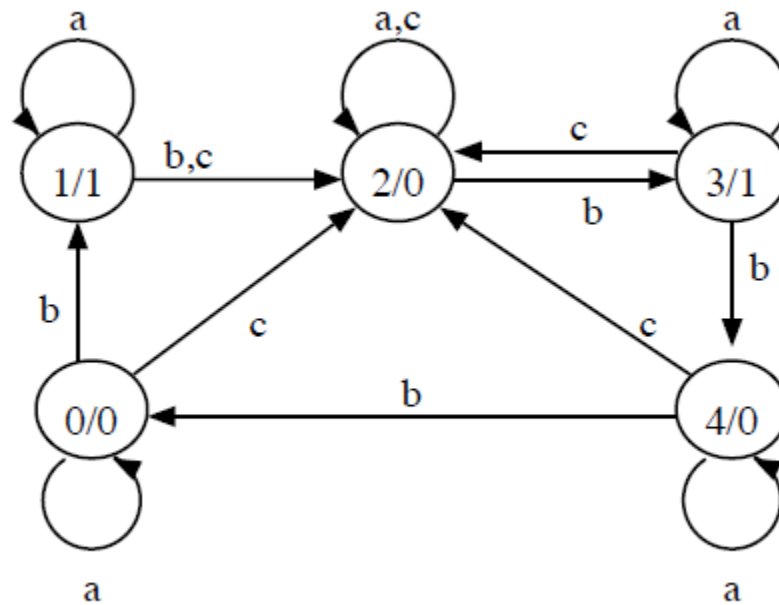

Ex7.15 Determine the minimal state table that is equivalent to the following:

	input	
PS	x=0	x=1
a	f, 0	b, 0
b	d, 0	c, 0
c	f, 0	e, 0
d	g, 1	a, 0
e	d, 0	c, 0
f	f, 1	b, 1
g	g, 0	h, 1
h	g, 1	a, 0
	NS, z	

### Exercise 7.15

From the state table we get

$$P_1 = (a, b, c, e)(d, h)(f)(g)$$

To obtain  $P_2$ , we determine the class of  $P_1$  to which the successors of the states belong.

	1 (a, b, c, e)	2 (d, h)	3 (f)	4 (g)
0	3 2 3 2	4 4	3	4
1	1 1 1 1	1 1	1	2

Thus,

$$P_2 = (a, c)(b, e)(d, h)(f)(g)$$

To obtain  $P_3$ , we determine the group of states of  $P_2$  to which the successors of the state belong.

	1 (a, c)	2 (b, e)	3 (d, h)	4 (f)	5 (g)
0	4 4	3 3	5 5	4	5
1	2 2	1 1	1 1	2	3

Therefore,  $P = P_3 = P_2 = (a, c)(b, e)(d, h)(f)(g)$  and the reduced table is

$PS$	$Input$	
	$x = 0$	$x = 1$
$a$	$f, 0$	$b, 0$
$b$	$d, 0$	$a, 0$
$d$	$g, 1$	$a, 0$
$f$	$f, 1$	$b, 1$
$g$	$g, 0$	$d, 1$
	$NS, Output$	

Ex7.17 Determine the minimal state table equivalent to the following one:

	Input			
PS	x=a	x=b	x=c	x=d
A	E, 1	C, 0	B, 1	E, 1
B	C, 0	F, 1	E, 1	B, 0
C	B, 1	A, 0	D, 1	F, 1
D	G, 0	F, 1	E, 1	B, 0
E	C, 0	F, 1	D, 1	E, 0
F	C, 1	F, 1	D, 0	H, 0
G	D, 1	A, 0	B, 1	F, 1
H	B, 1	C, 0	E, 1	F, 1
	NS, z			

**Exercise 7.17**

Based on the outputs for each state we get the first partition

$$P_1 = (A, C, G, H)(B, D, E)(F)$$

To obtain  $P_2$ , we determine the class of  $P_1$  to which the successors of the states belong.

	group 1				group 2			group 3
	<i>A</i>	<i>C</i>	<i>G</i>	<i>H</i>	<i>B</i>	<i>D</i>	<i>E</i>	<i>F</i>
<i>a</i>	2	2	2	2	1	1	1	
<i>b</i>	1	1	1	1	3	3	3	
<i>c</i>	2	2	2	2	2	2	2	
<i>d</i>	2	3	3	3	2	2	2	

Partition  $P_2$  is

	group 1	group 2			group 3			group 4
	<i>A</i>	<i>C</i>	<i>G</i>	<i>H</i>	<i>B</i>	<i>D</i>	<i>E</i>	<i>F</i>
<i>a</i>		3	3	3	2	2	2	
<i>b</i>		1	1	2	4	4	4	
<i>c</i>		3	3	3	3	3	3	
<i>d</i>		4	4	4	3	3	3	

Partition  $P_3$  is

	group 1 $A$	group 2 $C \quad G$	group 3 $H$	group 4 $B \quad D \quad E$	group 5 $F$
$a$		4    4		2    2    2	
$b$		1    1		5    5    5	
$c$		4    4		4    4    4	
$d$		5    5		4    4    4	

STOP.

The equivalent states are:  $\{A\}$ ,  $\{B,D,E\}$ ,  $\{C,G\}$ ,  $\{F\}$ ,  $\{H\}$

Minimal state transition table:

$PS$	$x = a$	$x = b$	$x = c$	$x = d$
$A$	$B/1$	$C/0$	$B/1$	$B/1$
$B$	$C/0$	$F/1$	$B/1$	$B/0$
$C$	$B/1$	$A/0$	$B/1$	$F/1$
$F$	$C/1$	$F/1$	$B/0$	$H/0$
$H$	$B/1$	$C/0$	$B/1$	$F/1$
	$NS/output$			